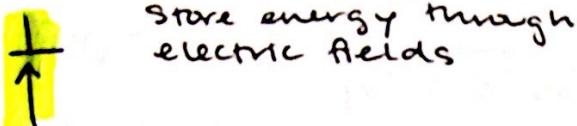


INDUCTANCE AND CAPACITANCE

→ Energy-storage Elements

CAPACITORS → C

- current through capacitor:

$$i_c = C \frac{dV_c}{dt}$$

- capacitors act as open circuits for steady state dc voltages
→ NO current

- C in series ⇒ R parallel

$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$

- capacitor problem ⇒ solve for voltage

- Units: farads [F]

- voltage does not change instantaneously

TRANSIENTS / SWITCHING

$$x(t) = x(\infty) + [x(0) - x(\infty)] e^{-t/\tau}$$

SS condition
after switch
flips

condition
just after
switch
flips

↑

$$\Rightarrow v(0^-) = v(0^+) = \underline{\underline{\text{SS before}}}$$

$\rightarrow R_{th}$ → resistance as seen through the capacitor as a load
capacitor:
 $x(t) \Rightarrow v(t)$

inductor:
 $x(t) \Rightarrow i(t)$

- voltage cannot change instantaneously across a capacitor

- To solve switching problems:

- ① make steady-state assumptions
- ② solve
- ③ flip the switch
- ④ solve

(AC) → surges

- current cannot change instantaneously across an inductor

$$v_o = \text{constant}$$

$$v(t) = A \sin(\omega t + \theta)$$

DC

AC

Time constant → measure of time to reach steady state

STEADY-STATE SINUSODIAL ANALYSIS → AC

$$V(t) = V_m \cos(\omega t + \theta)$$

peak value of the voltage (amplitude)
angular frequency (rad/s)
phase angle (degrees)

Sinusodial voltage

* To evaluate at a fixed time, convert θ to radians so you can evaluate $(\omega t + \theta)$

$$P(t) = \frac{V^2(t)}{R}$$

Power

$$E(t) = \int_0^T P(t) dt$$

energy of one period of oscillation

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$P_{avg} = \frac{V_{rms}^2}{R}$$

Average Power

$$P_{avg} = I_{rms}^2 R$$

$\omega \rightarrow$ natural freq.
 $f \rightarrow$ driving frequency
 $\omega = 2\pi f$ $f = \frac{1}{T}$
↳ [Hz]

$$\sin(\theta) = \cos(\theta - 90^\circ)$$

↳ Sinusodial function is normally expressed using cosine

Ex: $V_x(t) = 10 \sin(200t + 30^\circ)$
 $V_x(t) = 10 \cos(200t + 30^\circ - 90^\circ)$
 $= 10 \cos(200t - 60^\circ)$

* PHASORS: vector in the complex-number plane ⇒ transform function that represent sinusoidal voltages or currents

$$\Rightarrow V(t) = V_m \cos(\omega t + \theta)$$

$$\Rightarrow \bar{V} = V_m \angle \theta$$

$$V \cos(\omega t + \theta) = \bar{V} \angle \theta = V \cos \theta + j V \sin \theta$$

* phasors make equations not in the time domain
transform function (phasor)

* Impedance:

$$Z_L = j\omega L$$

[inductor \uparrow] lags

$$Z_C = -\frac{j}{\omega C}$$

[capacitor \uparrow] leads

$$Z_R = R$$

[resistor]

• Ohm's Law in the complex domain:

$$V = IR \Rightarrow V = (Z)I$$

• NOTES: $(\angle \theta_1)(\angle \theta_2) = \angle (\theta_1 + \theta_2)$

$$\frac{\angle \theta_1}{\angle \theta_2} = \angle (\theta_1 - \theta_2) \quad j = \angle 90^\circ$$

Impedance = Resistance in phasor domain

Norton-Thevenin, Mesh Analysis, Nodal Analysis, KVL, KCL, Ohm's Law ⇒ Still Apply!!!


$C \angle \theta = A + jB$

Polar rectangular

Mult/div ⇒ Polar Form
Add/sub ⇒ Rectangular Form

$$C = \sqrt{A^2 + B^2}$$
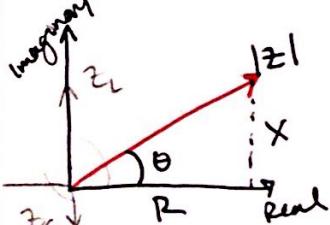
$$\theta = \tan^{-1}\left(\frac{B}{A}\right)$$



- capacitance → current leads voltage by 90°
- resistance → voltage is in phase with current
- inductance → current lags voltage by 90°


R = real part of impedance

X = imaginary part of impedance
 $[-\frac{j}{\omega C} \text{ or } j\omega L]$

$$Z = R + jX$$

real imaginary

Circuit Analysis

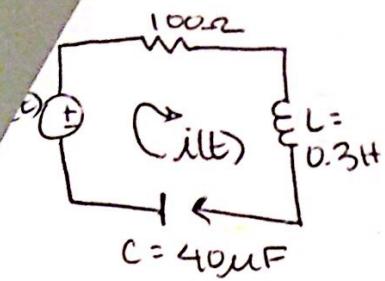

$$\begin{aligned} \bar{V}_s &= 100 \angle 30^\circ \\ &\quad \text{Circuit diagram: } R = 100\Omega, V_R, I, V_L, +j150\Omega, -j50\Omega, V_C \\ Z_{eq} &= Z_L + Z_C + R \\ &= 100 + j150 - j50 = 100 + j100 \\ &= 141.4 \angle 45^\circ \end{aligned}$$

① Replace time descriptions of sources with phasors (sources must have the same frequency)

② Replace inductances + capacitances with their complex impedances

$$Z_L = j\omega L = \omega L \angle 90^\circ$$

$$Z_C = -\frac{j}{\omega C}$$

$$\bar{I} = \frac{\bar{V}_s}{Z} = \frac{100 \angle 30^\circ}{141.4 \angle 45^\circ} = 0.707 \angle -15^\circ \rightarrow i(t) = 0.707 \cos(500t - 15^\circ)$$

You can find voltage across each element too $\rightarrow V_R = R \times I = 100 \times 0.707 \angle -15^\circ = 70.7 \angle -15^\circ$

POWER

$$P = V I$$

Power for general loads $\Rightarrow \frac{1}{2}, \frac{1}{4}, \frac{1}{8}, \frac{1}{16}$

$$V(t) = V_m \cos(\omega t)$$

$$i(t) = I_m \cos(\omega t - \theta)$$

$$P(t) = V_m I_m \cos(\omega t) \cos(\omega t - \theta)$$

$$(Q = V_{rms} I_{rms} \sin(\theta)) \quad \text{Reactive Power}$$

$$\text{Apparent power} = V_{rms} I_{rms} \sqrt{S} \quad \text{Apparent Power}$$

$$[Q] = [VATs]$$

$$[\text{app. power}] = [\text{volt-amperes (VA)}]$$

$$P^2 + Q^2 = (V_{rms} I_{rms})^2$$

$$S = P + jQ$$

complex power | APPARENT power
Real power, Avg. power, P-power, P → $\frac{1}{2}$
Reactive Power, Imaginary power, P → $\frac{1}{4}$

$Q (+)$ \Rightarrow Inductors

$Q (-)$ \Rightarrow Capacitors

$$P = \frac{V_m I_m}{2} \cos(\theta)$$

$$P = V_{rms} I_{rms} \cos(\theta)$$


Average Power units [W] watts

$\cos(\theta) \rightarrow$ power factor

$$= \cos(\theta_V - \theta_i)$$

$\theta \rightarrow$ power angle $(\theta_V - \theta_i) = \theta$

Power Triangle:

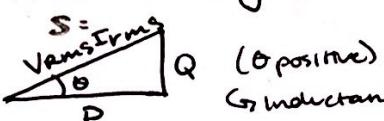

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$Z = R + jX$$

$$S = P + jQ$$

$$P_{app} = \sqrt{P^2 + Q^2} = |S|$$

$$P = \frac{V_{rms}^2}{R} = I_{rms}^2 R$$

$$Q = \frac{V_{rms}^2}{X} = I_{rms}^2 X$$

$$\mu \rightarrow 10^{-6}$$

$$P = \left(\frac{I}{\sqrt{2}}\right)^2 R = \frac{I^2}{2} R$$

ECE 83: Intro. To Electrical Engineering

Spring 2014
[EXAM #1]

3 MAIN CONCEPTS

① current = flow of electrons

[A]

② voltage = energy transferred; "potential energy"

[V]

③ resistance = "friction"

[Ω]

- fluid-flow analogy: current is a measure of the flow of charge through the cross section of a circuit element; voltage is measured across the ends of a circuit element, or between any two points in a circuit.

SOURCES

12V  Independent Voltage source

2A  Independent current source

4Vx  Dependent voltage source

- voltage-controlled voltage source
- current-controlled voltage source

2ix  Dependent current source

- voltage-controlled current source
- current-controlled current source

} these sources depend on something else in the circuit

KIRCHHOFF'S CURRENT LAW

• KCL: the net current (i) entering a node is zero.

→ to compute net current: add currents leaving a node and subtract currents entering

→ assume all unknown currents leave the node (+)

• Use Nodal Analysis to add currents and solve for voltages at nodes

(a) choose reference node ($V_g=0$), or ground node

(b) Assume all unknown currents leave the node
(if you get a negative result, you know the current actually enters the node)

(c) write KCL equations


(d) note: node voltages do not exist - they are mathematical constructs

* often it's useful to put ground node on (-) side of 


$$V_1 - V_2 + \frac{V_1 - V_3}{R_{12}} = 0$$

KIRCHHOFF'S VOLTAGE LAW

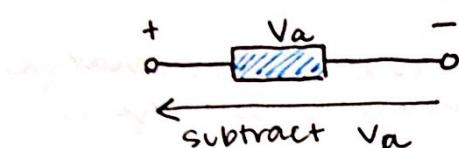- **KVL:** The sum of the voltages equals zero for any closed path (loop) in an electrical circuit
- Use Mesh Analysis of currents to solve for voltages
 - (a) identify loops in the circuit
 - (b) write and solve KVL equations for each constructed I-loop
 - * draw each loop in the same direction (clockwise)
- NOTE: add Va → $R_1(I_1 - I_2) + R_2(I_1) + V = 0$



POWER

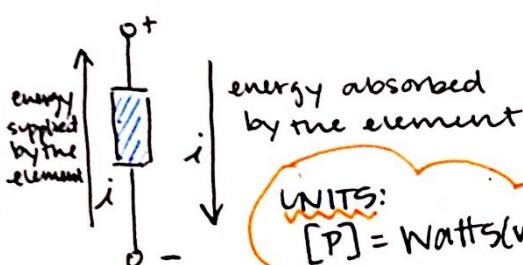

UNITS:
 $[P] = \text{Watts (W)}$
 $= \text{Volts} \times \text{Amperes}$

$$\text{Power} = \text{Voltage} \times \text{current}$$


$$P = VI$$

$$P = Vi = i^2 R = \frac{V^2}{R}$$

- resistors always dissipate (absorb) power
- sources may dissipate or supply power
 - if current enters (-) side → supply power!
 - current enters (+) side → dissipate!

CIRCUITS

SERIES CIRCUIT

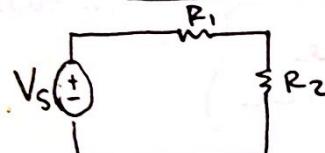

- current is the same through resistors in series
- voltage changes

* **Voltage divider**

$$V_1 = \left(\frac{R_1}{R_1+R_2} \right) V_s$$


* $(R_{\text{eq}})_{\text{series}}$

$$(R_{\text{eq}})_{\text{series}} = \sum_{i=1}^n R_i$$

↳ add up resistances for resistors in series

vs.

PARALLEL CIRCUIT

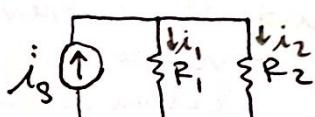

- current splits
- voltage is the same for elements in parallel

* **Current divider**

$$i_2 = \left(\frac{R_2}{R_1+R_2} \right) i_s$$


* $(R_{\text{eq}})_{\text{II}}$

$$(R_{\text{eq}})_{\text{II}} = \frac{R_1 R_2}{R_1+R_2}$$

S LAW

$$V = iR$$

- **Resistors:**

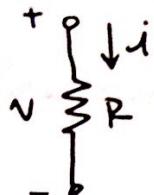

- Ohm's Law relates voltage and current
- usually applied after KCL or KVL for solving problems


- current moves from higher to lower potential through resistors - always! (i.e. 10V to 5V)
- current travels the path of least resistance

SUBCIRCUITS

- goal → simplify circuits
- lens: what are we looking through? (usually a $\frac{1}{j}$)
- neglect the lens element in analysis of circuit
- Open circuit: no current flow
- Short circuit: current flows, but no voltage (connected by an ideal conductor)


THEVENIN SUBCIRCUIT

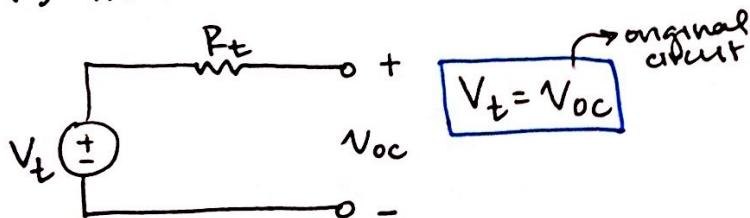- consists of an independent V_t in series with a resistance R_t



NORTON SUBCIRCUIT

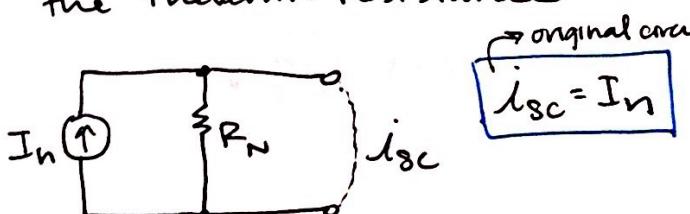- consists of an independent current source I_{sc} in parallel with the Thevenin resistance




• use short circuit to get rid of parallel resistor

- If and only if, you have no dependent sources, you can solve for R_t directly by zeroing out sources

$\oplus \Rightarrow SC$

$\ominus \Rightarrow OC$

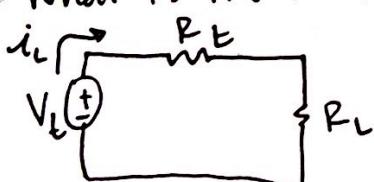- We can replace any circuit with a Thevenin or Norton equivalent
- What is the maximum power across the resistor?



if $R_L = R_t \dots$

$$P_{max} = \frac{V_t^2}{4R_t}$$

requirement for max. power!

Source Transformation!

- to find a \oplus or \ominus equivalent, you need to find 2 of the following 3:

$$V_t, I_N, R_t \quad \text{or} \quad i_{sc}, V_{oc}, R_t$$

- Steps to Solve:

1) zero out sources to solve for $R_{eq} = R_t = R_N$


2) go back to original circuit w/ sources to solve for one other variable

- You can replace Norton w/ Thevenin (or opposite) to solve problems!

EXAMPLE PROBLEMS

-VL

Find V.

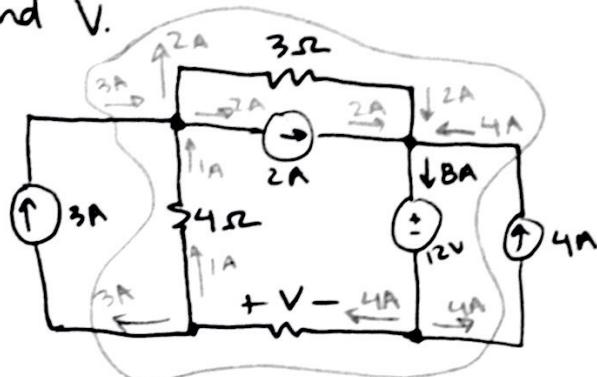

$$V = IR$$

$$[V] = [R][I]$$

• observe circuit to add currents


• KVL of loop

$$(4\Omega)(1A) + (3\Omega)(2A) + 12V - V = 0$$

$$4 + 12 + 12 = V = 22V$$

NODAL ANALYSIS (KCL)

Find V.

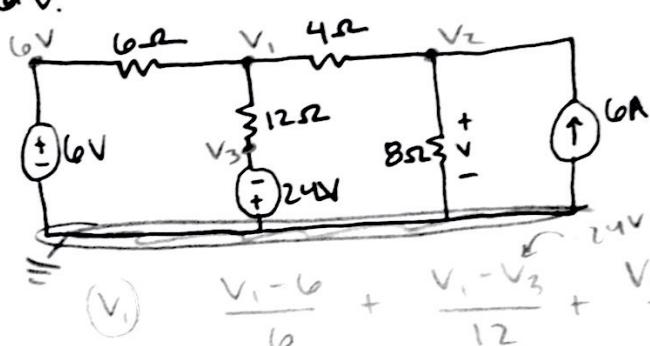

- choose ground node on (-) side of (+) to give voltage at a node
- (+) voltages leaving node

$$V_1 = 9V$$

$$V_2 = 22V$$


$$(V_1) \frac{V_1 - 6}{6} + \frac{V_1 - V_3}{12} + \frac{V_1 - V_2}{4} = 0$$

$$V = V_2 = 22V$$

$$(V_2) V_3 = -24V$$

MESH ANALYSIS (KVL)

Find $i_{3,52}$.

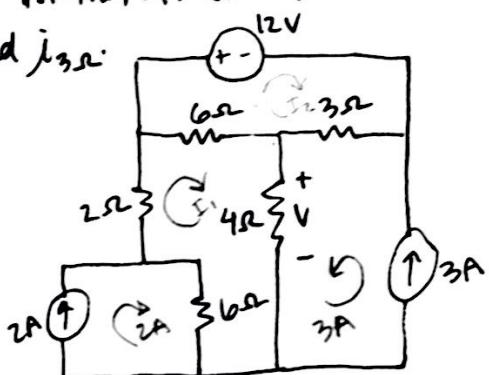

$$\text{mesh } I_1: 2I_1 + 6(I_1 - I_2) + 4(I_1 + 3) + 6(I_1 - 2) = 0$$


$$\text{mesh } I_2: 3(I_2 + 3) + 6(3 - I_1) + 12V = 0$$

$$\begin{aligned} & 9I_2 - 6I_1 = 21 \rightarrow I_1 = 1A \\ & -6I_2 + 18I_1 = 0 \quad \rightarrow I_2 = -3A \end{aligned}$$

$$i_{3,52} = I_2 + 3 = 0$$

NORTON (THEVENIN)

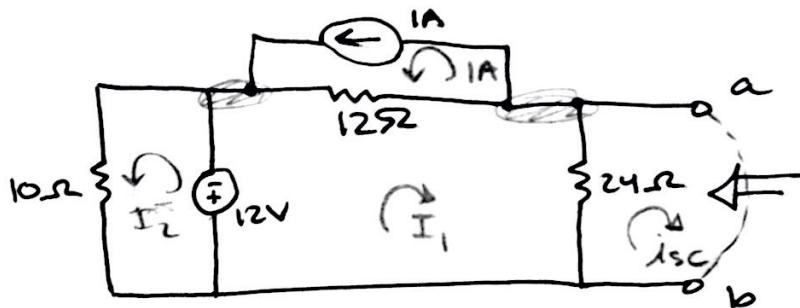
Find the Norton & Thevenin equivalent subcircuits



- no $\Delta \rightarrow$ zero at sources
- $\oplus \rightarrow$ SC
- $\ominus \rightarrow$ OC
- go back to original circuit to find I_{SC} or V_{OC}

$$R_{eq} = R_t = \frac{12}{12+24} = \frac{(12)(24)}{12+24} = 8\Omega$$

• Mesh Analysis

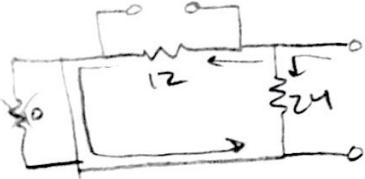

Mesh I_{SC} : $24(I_{SC} - I_1) = 0$

Mesh I_1 : $24(I_1 - I_{SC}) + 12 + 12(I_1 + I) = 0$
 $\hookrightarrow 24I_1 - 24I_{SC} + 24 + 12I_1 = 0$

$$I_{SC} = -2A \quad \rightarrow \quad I_N = I_{SC} \quad V_t = I_{SC} R_t$$

