

LEHIGH UNIVERSITY
DEPT. OF ELECTRICAL & COMPUTER ENGINEERING

ECE 083 – INTRODUCTION TO ELECTRICAL ENGINEERING

SPRING 2010




FINAL EXAMINATION



Problem #1 (5)

Find i_{10} and V_5

For the given Circuit

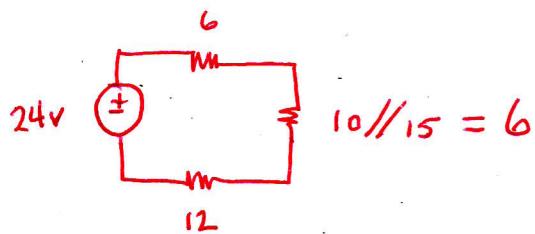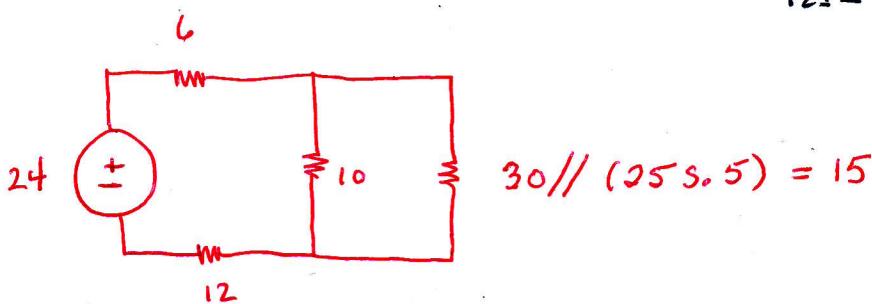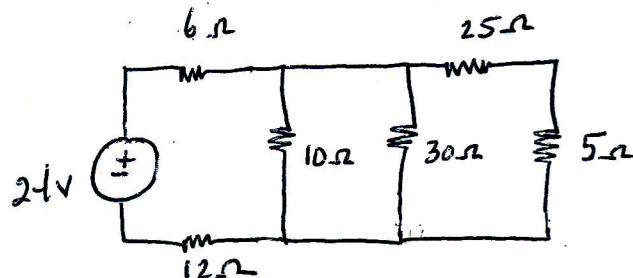


$$24V \parallel 6\Omega = 24 \quad \text{Hence } i = 1A$$

$$\text{By Current Division : } i_{10} = \frac{15}{10+15} (1) \Rightarrow \boxed{i_{10} = 0.6A}$$


By Observation, Non "Parallel Elements," $\boxed{V_5 = 1V}$
Ans Voltage Division \Rightarrow

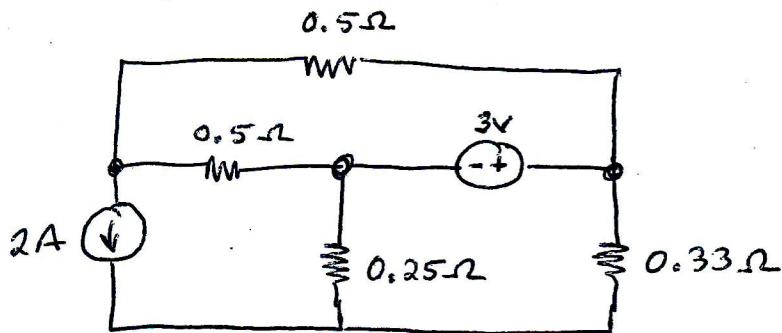Problem # 2 (10)

Find the Current through the Voltage Source For the Following Circuit



We Will Use "Mesh Analysis"

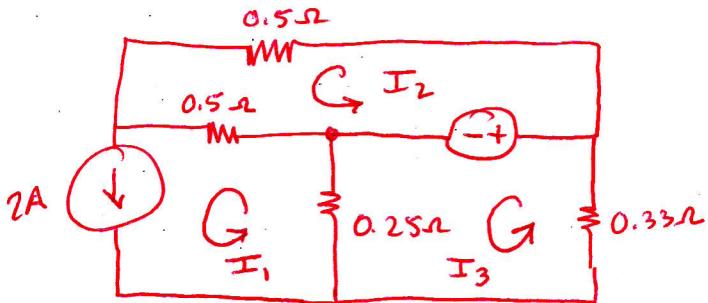

$$\underline{\text{Note}} : I_1 = 2 \text{ A}$$

$$\text{Mesh } I_3 : 0.33 I_3 + 3 + (I_3 - 2) = 0$$

$$\text{Mesh } I_2 : 0.5 I_2 + 0.5 (I_2 - 2) - 3 = 0$$

$$\text{Solving} : I_3 = -4.31 \text{ A}$$


$$I_2 = 4 \text{ A}$$

$$\text{Hence } i_{\text{top}} = 4.31 \text{ A} + 4 \text{ A}$$

$$\boxed{\sum i_{\text{top}} = 8.31 \text{ A} \rightarrow}$$

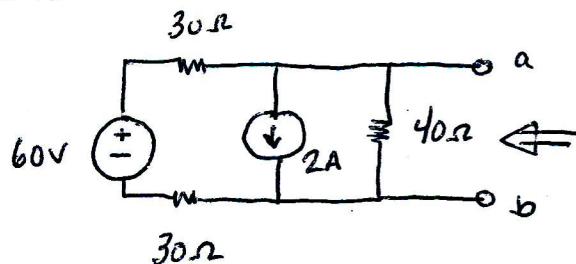Problem # 3 (15)


Find the Norton and Thevenin Circuits
For the Following Circuit.



No Dependent Sources ... Zero Out Sources ($\oplus = \text{OC}$, $\ominus = \text{SC}$) And
Solve For R_{TH} Directly.

$$R_{\text{TH}} = 40 \parallel 30 \text{ s. } 30 \Rightarrow \boxed{R_{\text{TH}} = 24 \Omega}$$

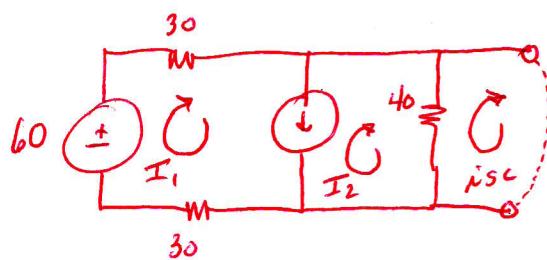We Will Use Mesh + Noting that We Never Write A Mesh Equation For Anything
that Will Contain A Current Source (Unknown V). Then Solve For i_{sc}



(Wors: Units V, Ω)


$$30 I_1 + 40 (I_2 - i_{\text{sc}}) + 30 I_1 = 60$$

$$40 (i_{\text{sc}} - I_2) = 0$$


$$I_1 - I_2 = 2 \quad (\text{compatibility relationship})$$

Solving: $i_{\text{sc}} = 1 \text{ A} \uparrow$

Hence:

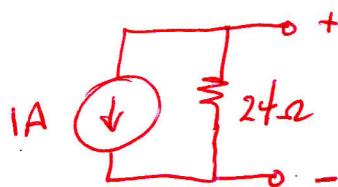

(N)

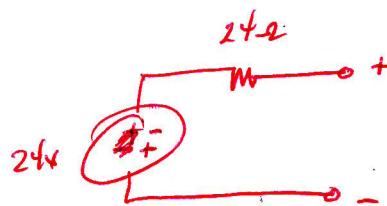

(T)

Problem # 4 (10)


For the Following Set of Equations
Construct the Corresponding Circuit

$$\frac{V_1 - V_2}{10} + \frac{V_1 - V_3}{10 - j^{20}} = 0 \quad (1)$$

$$\frac{V_2 - V_1}{10} + \frac{V_2}{j^{10}} + \frac{V_2 - V_3}{j^{40}} = 0 \quad (2)$$

$$\frac{V_3 - V_1}{10 - j^{20}} + \frac{V_3 - V_2}{j^{40}} = -20 \quad (3)$$

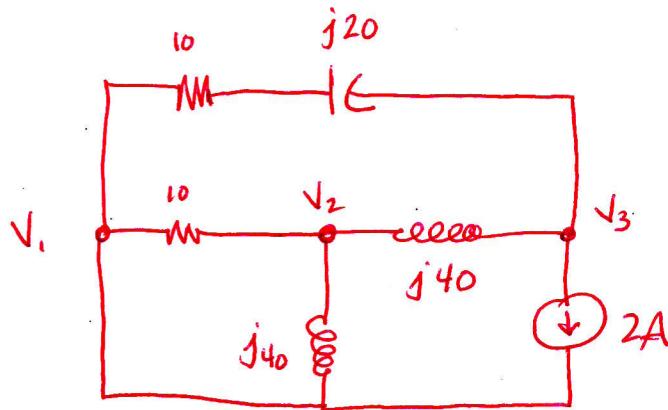There Are Several Solutions to This Problem. Below is Just One of Them.



Note: With w Not Given We Can Only Set This Up
Using Impedance Values

Problem # 5 ⑤

Find $V_s(t) = V_1(t) + V_2(t)$

IF $V_1(t) = 10 \cos(\omega t - 30^\circ)$

$V_2(t) = 15 \sin(\omega t + 60^\circ)$

$V_1 = 10 \cos(\omega t - 30^\circ)$

$V_2 = 15 \cos(\omega t - 30^\circ)$ [Note: $\sin \rightarrow \cos$ transform]

$V_1 = 10 \angle -30^\circ = 10(\cos 30^\circ - j \sin 30^\circ) = 8.66 - j 5$

$V_2 = 15 \angle -30^\circ = 15(\cos 30^\circ - j \sin 30^\circ) = 12.99 - j 7.5$

Since ω is the same for both signals :

$$V_1(t) + V_2(t) = 21.65 - j 12.5$$

$$= \sqrt{21.65^2 + 12.5^2} \angle \tan^{-1}\left(\frac{-12.5}{21.65}\right)$$

$$= 25 \angle -30^\circ$$

$\{V_s(t) = 25 \cos(\omega t - 30^\circ)\}$

Note: We could have noted this at the beginning since both $V_1(t) \& V_2(t)$ have same ω and θ so they could have been just added!


Problem # 6 (20)

For the Following Circuit

Find V_s , i_1 , i_2 , and i_3

Let $i_s = 8 \cos(200,000t) A$
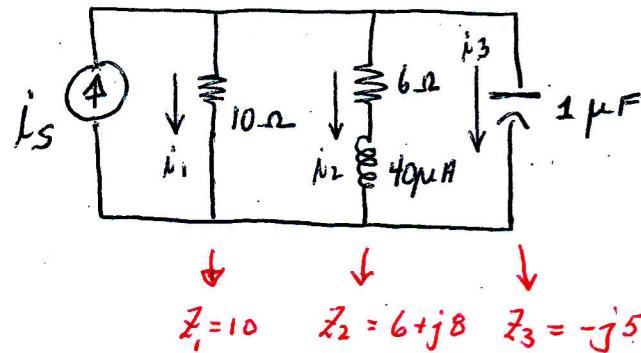
$$i_s = 8 \angle 0^\circ \text{ with } \omega = 200,000$$



Note: $Z_R = R$, $Z_L = j\omega L$, $Z_C = \frac{-j}{\omega C}$

Hence $\boxed{Z_{eq} = 5 \angle -36.8^\circ}$

Then $V_s = (8 \angle 0^\circ)(5 \angle -36.8^\circ) = 40 \angle -36.8^\circ$

$\boxed{V_s(t) = 40 \cos(200,000t - 36.8^\circ)}$

Then $i_1 = \frac{V_s(t)}{10} \Rightarrow i_1 = \frac{40 \angle -36.8^\circ}{10} = 4 \angle -36.8^\circ \Rightarrow \boxed{i_1 = 4 \cos(200,000t - 36.8^\circ)}$


$$i_2 = \frac{V_s(t)}{6+j8} = \frac{40 \angle -36.8^\circ}{10 \angle 53.1^\circ} = 4 \angle -90^\circ \Rightarrow \boxed{i_2 = 4 \cos(200,000t - 90^\circ)}$$

$$i_3 = \frac{V_s(t)}{-j5} = \frac{40 \angle -36.8^\circ}{5 \angle -90^\circ} = 8 \angle 53.2^\circ \Rightarrow \boxed{i_3 = 8 \cos(200,000t + 53.2^\circ)}$$

Note: If you Add $i_1 + i_2 + i_3$ you will arrive at $\underline{i_s = 8 \angle 0^\circ}$
Nice Check!

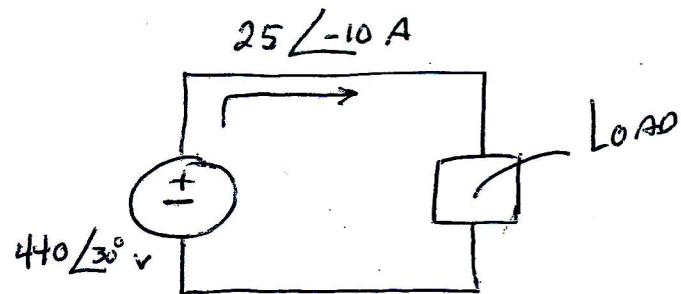Problem #7 (10)

Determine the Real Power, Complex Power, reactive Power and Apparent Power Absorbed by the load. Also, find the PF for the load



$$V_{rms} = \frac{440}{\sqrt{2}} = 311.13 \text{ V} \quad I_{rms} = \frac{25}{\sqrt{2}} = 17.68 \text{ A} \quad \theta = (\theta_r - \theta_i) = 40^\circ$$

$$P_{avg} = P_{real} = V_{rms} I_{rms} \cos(\theta) = \underline{\underline{4213.2 \text{ W}}}$$

$$Q = P_{reactive} = V_{rms} I_{rms} \sin(\theta) = \underline{\underline{3535.33 \text{ VAR}}}$$

$$P_{app} = V_{rms} I_{rms} = 5500 \text{ VA}$$

$$\text{pf} = \cos \theta = .766 \text{ or } 76.6\%$$

$$\begin{aligned} S_{\text{complex}} &= P_{\text{real}} + j P_{\text{reactive}} \\ &= P_{\text{real}} + j Q \\ &= 4213.2 + j 3535.33 \\ &= 5500 \angle 40^\circ \end{aligned}$$

Note: This checks with P_{app} & θ !

Problem # 8 (15)


An Input Signal given By

Signals Have
Different W.
Must Analyze
Separately !!

$$V_{in}(t) = 3 + 4\cos(1000\pi t) + 5\cos(2000\pi t - 30^\circ)$$

is Applied to an RL Circuit As shown.

Find the Output Signal.

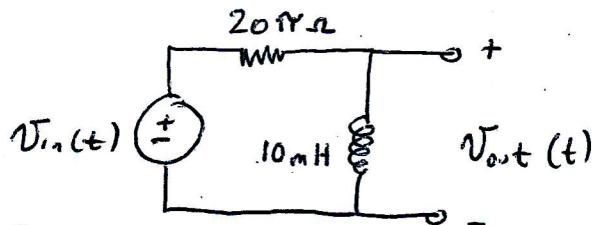

Analyzing this Circuit We See this is A
First-Order High Pass Filter.

$$\text{Hence : } |H(f)| = \frac{f/f_B}{\sqrt{1 + (f/f_B)^2}} \quad \text{and} \quad f_B = \frac{R}{2\pi L} = 1000 \text{ Hz}$$

$$\textcircled{1} \omega = 0 \rightarrow f = 0$$

$$|H(0)| = 0 \quad \angle H(0) = 0 \quad \Rightarrow \quad \text{Note: This Makes Sense As We See that A HPF Will Allow A DC Signal Pass}$$

$$\textcircled{2} \omega = 1000 \rightarrow f = 500$$

$$|H(500)| = 0.447 \quad \angle H(500) = 63.43^\circ$$


$$\textcircled{3} \omega = 2000 \rightarrow f = 1000$$

$$|H(1000)| = 0.707 \angle 45^\circ$$

$$\text{Hence: } V_{out} = (0)(3) + (0.447)(4)\cos(1000\pi t + 63.43^\circ) + (0.707)(5)\cos(2000\pi t + 15^\circ)$$

$$V_{out} = 1.79 \cos(1000\pi t + 63.43^\circ) + 3.53 \cos(2000\pi t + 15^\circ)$$

Problem #9 (10)

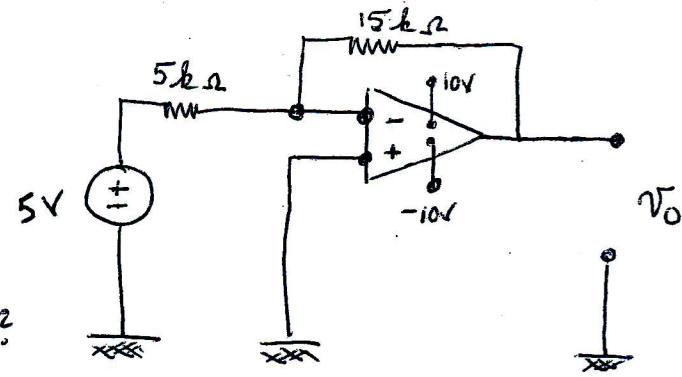

For the given circuit shown

1) what type of OP-Amp is this?

2) If we say this is ideal

what does this mean?

3) Calculate V_o

① This is A Schematic of An "Inverting" Amplifier

② For Our Purposes Ideal Means that The Summing-Point Constraint is Valid. This Means that $i_p = i_n = 0$ and $V_p = V_n$. Also Ideal Means that V_o must Lie Within "Voltage of Op-Amp".


③ Negative Feedback is Present

$$V_o = - \frac{15}{5} (5) = -15V$$

Hence this lies Outside the $\pm 10V$ Range So We Say that the Op-Amp is Saturated. Hence $\underline{V_o = -10V}$

Problem #10

Extra Credit {10 points}

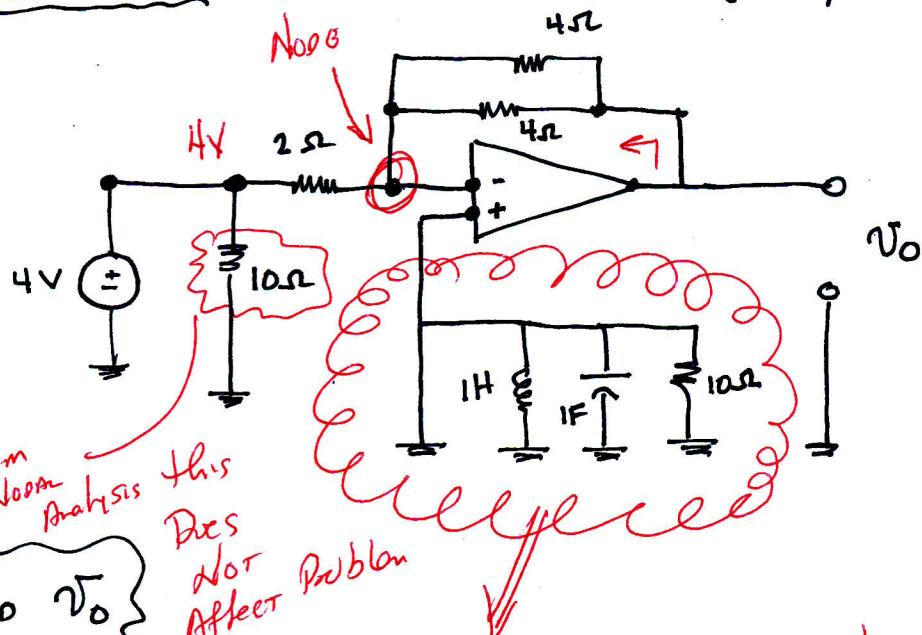

Please Observe these are grounds
 So Nothing Passes through them!
 They Do Not Affect the Op-Amp.

$$\text{KCL For Node: } \frac{4}{2} + \frac{V_o}{2} = 0$$



2 4Ω resistors

$$1n \parallel \Rightarrow R_{\text{eq}} = 2\Omega$$

$V_o = -4V$