

LEHIGH UNIVERSITY

**DEPT. OF ELECTRICAL & COMPUTER ENGINEERING
ECE 081 – PRINCIPLES OF ELECTRICAL ENGINEERING**

FALL 2010


MIDTERM EXAMINATION

WEDNESDAY 20 OCTOBER 2010

Problem #1

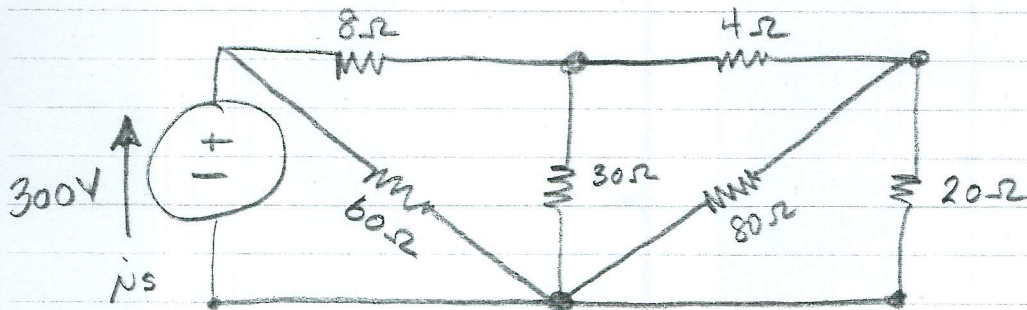(15)


For the Circuit Shown, Find i_s and the Power Dissipated By the $30\text{-}\Omega$ Resistor.



Problem #2

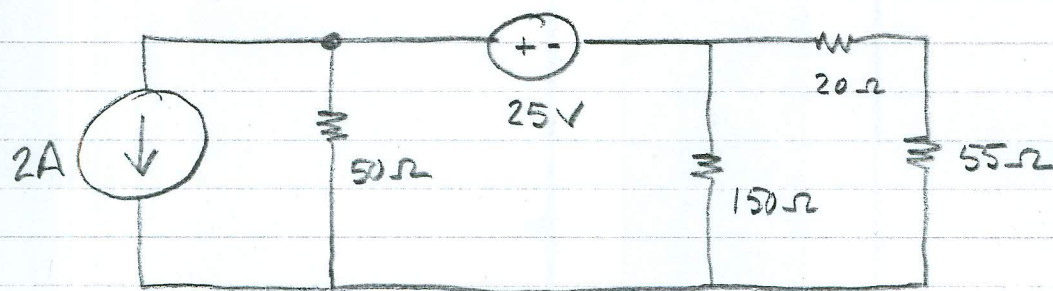(25)


For the Circuit Shown, Find the Power Delivered By the 2A Current Source.



Problem #3

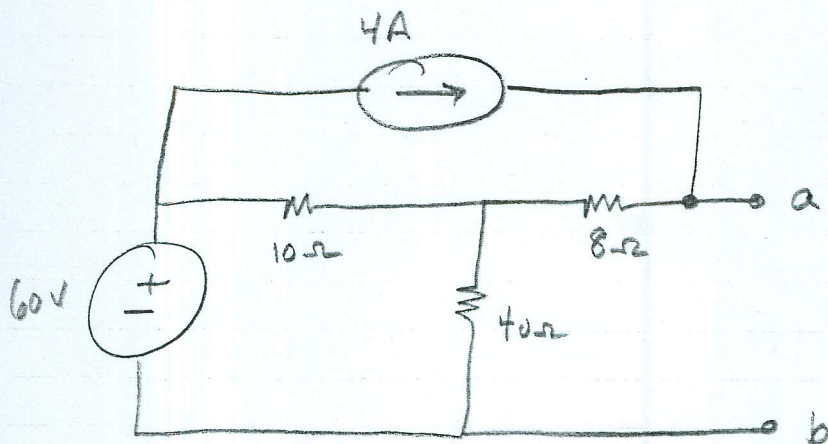(25)

For the Circuit Shown, Find the
N-T Subcircuits with respect to
the Terminals a-b.




Problem #4

(25)

For the Circuit Shown, Find :

$v_c(t)$ for $t \geq 0$ and $i_c(t)$ $t \geq 0$.

Note: BE EXTRA CAREFUL OF SIGNS !!

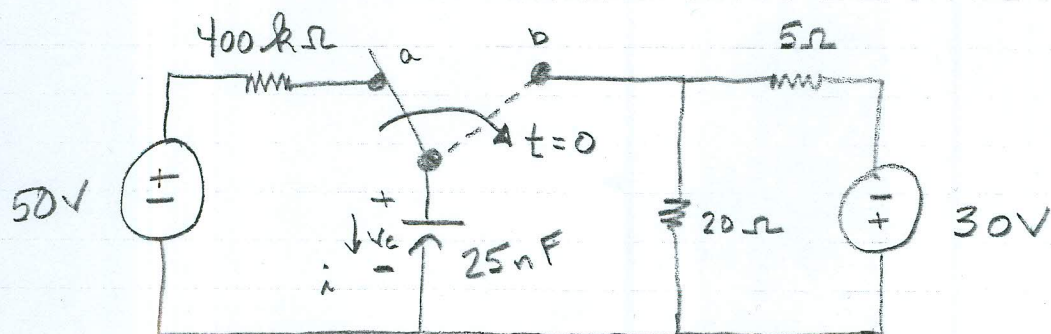

Note: At $t=0$
Switch flips
From $a \rightarrow b$

Problem #5


⑩

You Have A Collection Of Only 10Ω and 50Ω RESISTORS. You Need A Circuit Whose $R_{eq} = 87.5\Omega$. Design A Circuit That Will Accomplish This With the minimum Number Of RESISTORS.

EXAM SOLUTIONS

#1

Starting From Left Hand End:

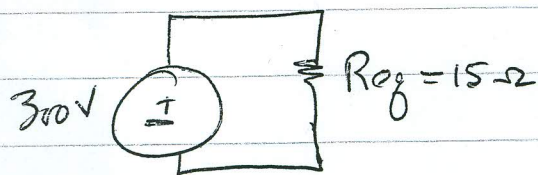

$$I_s = \frac{300V}{15\Omega} = \underline{\underline{20A}}$$


$$80 // 20 = 16$$

$$4S \cdot 16 = 20$$

$$30 // 20 = 12$$

$$8S \cdot 12 = 20$$
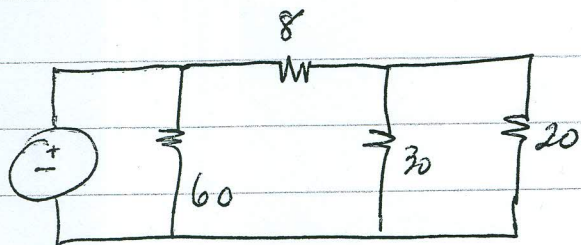
$$60 // 20 = \underline{\underline{15 = R_{eq}}}$$




$$I_{8\Omega} = \frac{60}{80} (20) = 15A$$

$$I_{30} = \frac{20}{50} (15) = 6A$$

$$P = I^2 R = (6)^2 (30) = \underline{\underline{1080W}}$$

#2

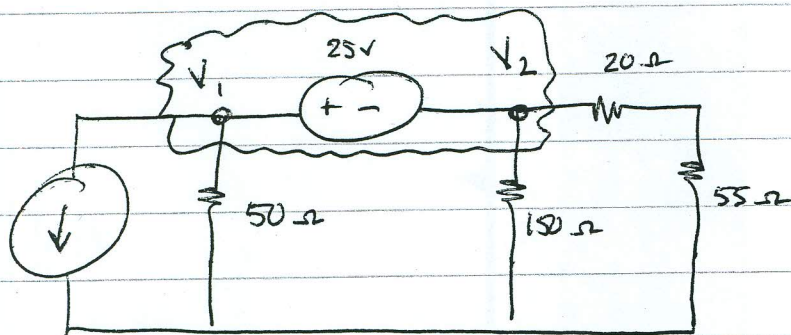

NOTE: $V_{\downarrow} = V_{20\Omega}$
(// Elements)

NOTE: $V_1 - (+) - V_2$

Form Supernodes


NOTE: $\frac{V_1}{50} + \frac{V_2}{150} + \frac{V_2}{75} + 2 = 0$

Continuing: $V_1 = V_2 + 25$



Solving: $V_1 = -37.5V$

Hence: $P_{\downarrow} = (I)(V)$
 $= (2)(-37.5)$
 $= -75W$
 (Delivered)
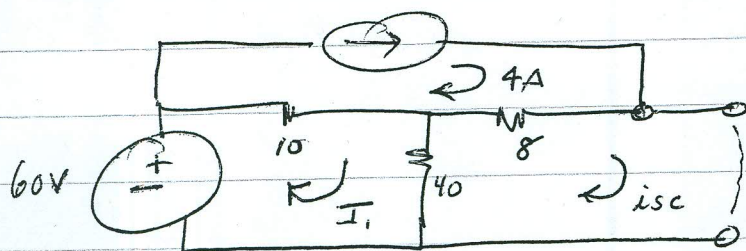
#3 Zero Out Sources : $R_{TH} = 8S. (10//40) = 16\Omega$


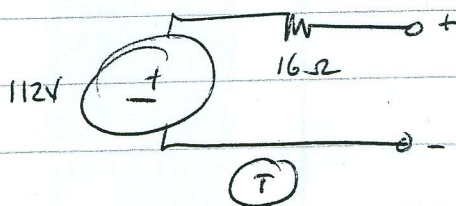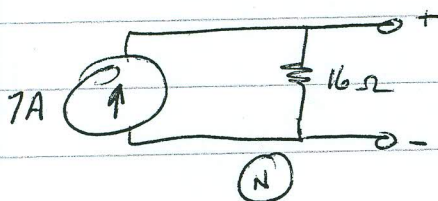
$$\begin{cases} \underline{I_1} : 10(I_1 - 4) + 40(I_1 - i_{sc}) - 60 = 0 \\ \underline{i_{sc}} : 40(i_{sc} - I_1) + 8(i_{sc} - 4) = 0 \end{cases} \quad \begin{cases} i_{sc} = 7A = I_N \\ V_{oc} = (R_T)(I_N) = 112V \end{cases}$$



#4 $V(0) = 50V$ (Note: With SS and OC No Current Flows through 40 ohm)

$V(\infty) = \frac{20}{25}(-30) = -24V$ (Note: Sign is - DUE TO (+) POLARITY)

$$R_{TH} = 5//20 = 4\Omega \quad \tau = R_{TH}C = 0.1\mu s \Rightarrow \frac{1}{\tau} = 10^7$$

$$V_c(t) = V(\infty) + [V(0) - V(\infty)]e^{-t/\tau}$$

$$V_c(t) = -24 + 74e^{-10^7 t}$$


$$i_c(t) = C \frac{dV_c}{dt} = 25 \times 10^{-9} (10^{-7}) (74e^{-10^7 t})$$

$$i_c(t) = -18.5e^{-10^7 t}$$

Note: It is Much More Difficult to Solve this Problem if You Look @ $i_c(0^-)$, $i_c(0^+)$ etc. Remember Dfns!!


#5

BEST :

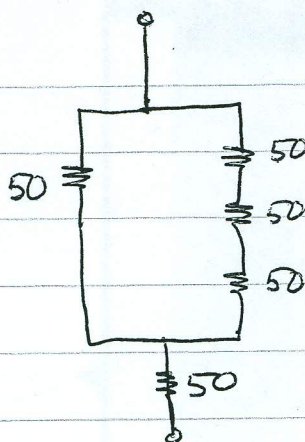


⑤ Resistors

BEST :

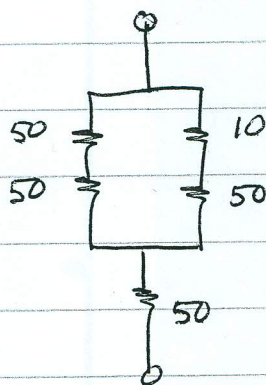

⑤ Resistors

STANDARD
(Acceptable) :

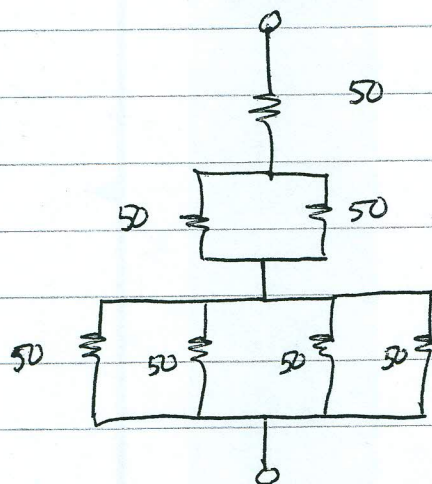

⑦ Resistors

Note : There are several other ⑦ Resistor combinations!