

LEHIGH UNIVERSITY

DEPT. OF ELECTRICAL & COMPUTER ENGINEERING

ECE 083 – INTRODUCTION TO ELECTRICAL ENGINEERING


SPRING 2010

EXAM #1

SOLUTIONS

#1 For the circuit shown find V

10

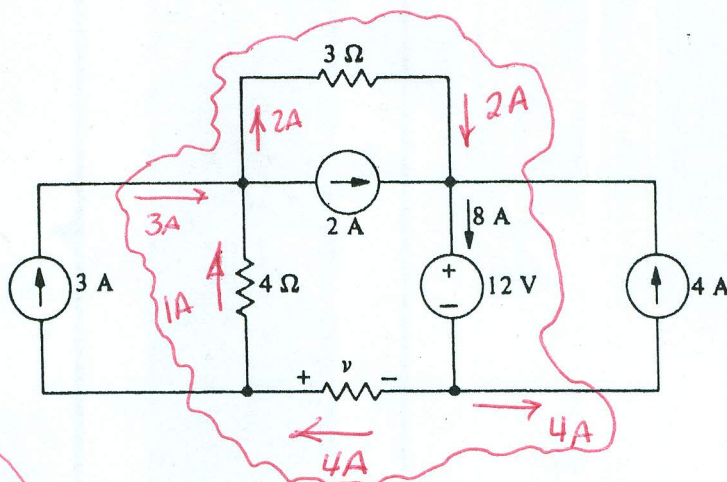

NOTE: Observing And
Analyzing Nodes We See

NOTE: KVL OF Loop Voids


$$6 + 12 - V + 4 = 0$$

$$V = 22V$$

#2

For the Given Circuit Find V

10

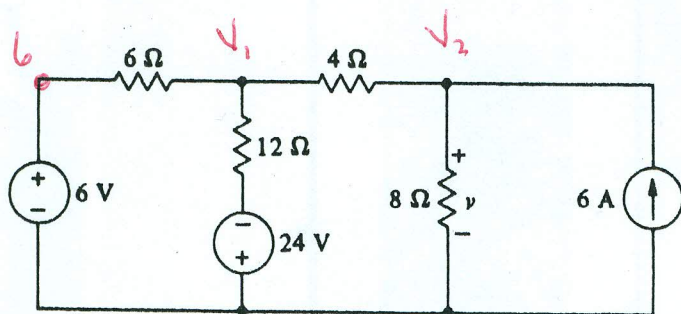

Using Node Voltages :

$$\frac{V_1 - 6}{6} + \frac{V_1 - V_2}{4} + \frac{V_1 + 24}{12} = 0$$

$$\frac{V_2 - V_1}{4} + \frac{V_2}{8} - 6 = 0$$

Solving These :

$$V_1 = 9V$$

$$V_2 = 22V$$


Hence : $V = V_2$

$$\boxed{V = 22V}$$

#3

For the Given Circuit Find $i_{3\Omega}$

20.

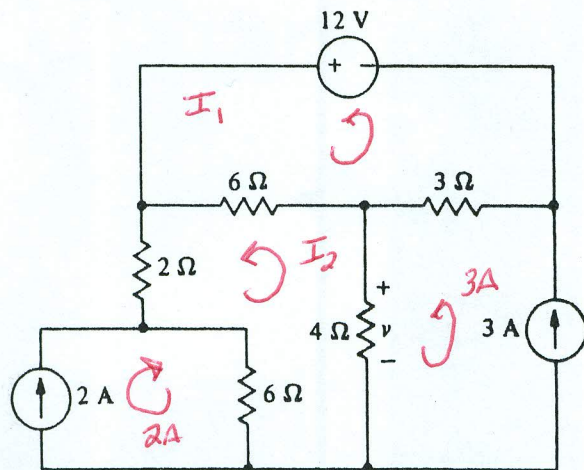

$$I_{1 \text{ mesh}} : -12 + 6(I_1 - I_2) + 3(I_1 - 3) = 0$$

$$I_{2 \text{ mesh}} : 6(I_2 - I_1) + 2(I_2) + 6(I_2 + 2) + 4(I_2 - 3) = 0$$

$$\begin{aligned} \text{These Become: } 9I_1 - 6I_2 &= 21 \\ -6I_1 + 18I_2 &= 0 \end{aligned}$$

$$\begin{aligned} \text{Solving } I_1 &= 3A \\ I_2 &= 1A \end{aligned}$$


$$\text{Hence: } i_{3\Omega} = I_1 - 3$$

$$i_{3\Omega} = 0$$

#4

Find the Norton & Thevenin Equivalent Subcircuits
For the following circuit.

25

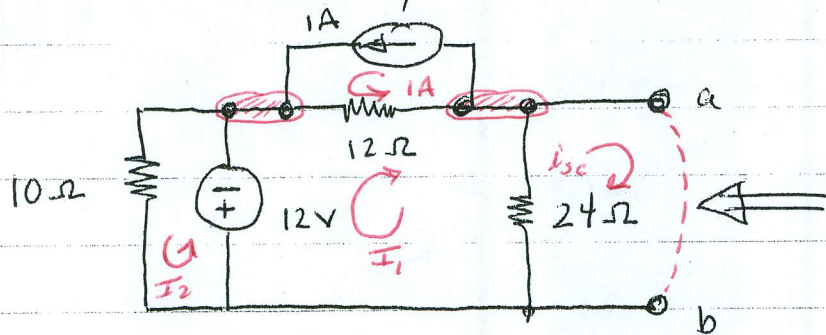


No Dependent Sources : Zero Sources (\downarrow DC, \oplus SC) and Solve Directly.

$$R_{TH} = 24 // 12 = 8\Omega \quad (\text{Note: Short Circuit } \oplus \text{ Connect Out } 10\Omega)$$

$$i_{sc} : 24(i_{sc} - I_1) = 0$$

$$I_1 : 24(I_1 - i_{sc}) + 12 + 12(I_1 + 1) = 0$$

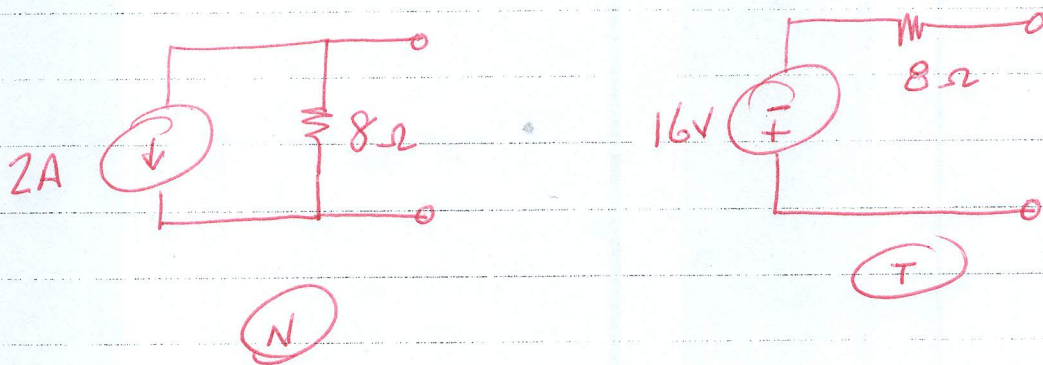
Solving: $\{i_{sc} = -2A\} \Rightarrow I_N = i_{sc} \quad V_T = i_{sc} R_{TH}$



#5

Find $i(t)$ for $t > 0$ if the circuit is in
Steady State Prior to the Switch Moving From
① to ②

25

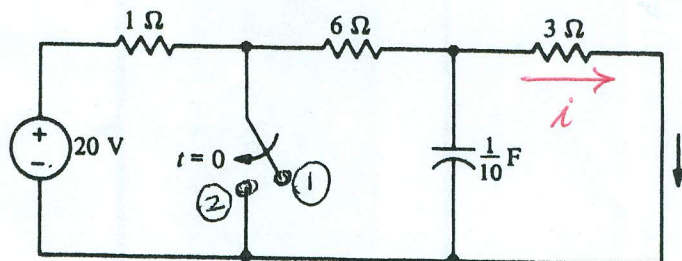

In Steady State: $\frac{1}{s}$ Act As Open Circuits

$$i(0) = \frac{20}{10} = 2A \quad (\text{With } \frac{1}{s} \text{ oc } R_{eq} = 1 + 5 + 3 = 9)$$

After Switch Closes No Current or Voltage Will Reach i_{ss} .

Hence $i(\infty) = 0A$

From our Definition: $i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$

But $\tau = R_{TH} C$

↓
As Seen through
the Capacitor

$$i(t) = 0 + [2 - 0]e^{-t/2}$$

$$R_{TH} = 6//3$$

$$= 2$$

$$i(t) = 2e^{-5t}$$

$$\tau = 2\left(\frac{1}{10}\right) = 0.2$$

- #6 You Have A Collection Of Only 50Ω and 10Ω resistors.
You Need A Circuit whose $R_{eq} = 87.5\Omega$. Design
10 A Circuit that Accomplishes this With the Minimum
Number of resistors.

$$87.5\Omega = 50 + 25 + 12.5$$

