

Lough University

Department of Electrical Engineering

LCE 083 - Spring 2009

Exam #2


8 April 2009

SOLUTIONS

Problem #1:

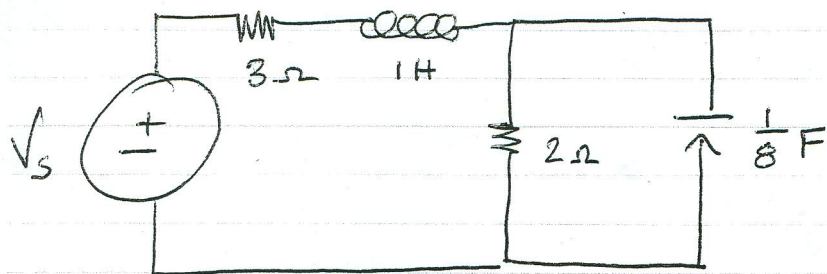(10)

Find The Current i For the Following Circuit.



$$V_s = 10 \cos 4t \text{ V}$$

$$\omega = 4$$

$$j\omega L = j4$$

$$\frac{-j}{\omega C} = \frac{-j}{4(\frac{1}{8})} = -j2$$

$$2 // -j2 = \frac{-j4}{2-j2}$$

$$3 + j4 - \frac{j4}{2-j2} = Z_{eq} = \frac{14-j2}{2-j2} = \frac{14.1 \angle -8.1}{2.8 \angle -45} = 5 \angle 36.9 = Z_{eq}$$

$$\bar{I} = \frac{\bar{V}}{Z} = \frac{10}{5 \angle 36.9} = 2 \angle -36.9$$

$$i(t) = 2 \cos(4t - 36.9) \quad (*)$$

Problem #2:

(10)

Consider A Load that has An Impedance Value of $\bar{Z} = 100 - j50 \Omega$. The Current Passing through the Load is $\bar{I} = 25\sqrt{2} \angle 45^\circ$. Is the Load Capacitive or Inductive? Determine the Power, Power Factor, Reactive Power, Apparent Power and Power Angle Delivered to the Load.

$$\bar{Z} = 100 - j50 \Rightarrow \bar{Z} = 111.8 \angle -26.56$$

$$\bar{I} = 25\sqrt{2} \angle 45^\circ \Rightarrow \bar{I}_{rms} = 25 \angle 45^\circ$$

Capacitive since j term is negative

$$P = (\bar{I}_{rms})^2 R = (25)^2 (100) = 62.500 \text{ W} = 62.5 \text{ kW}$$

$$Q = (\bar{I}_{rms})^2 X = (25)^2 (-50) = -31.250 \text{ VAR} = -31.25 \text{ kVAR}$$

$$P_{app} = \sqrt{P^2 + Q^2} = 69.87 \text{ kVA}$$


$$V_{rms} = I_{rms} Z_{rms} = [118.8 \angle -26.5^\circ] [25 \angle 45^\circ] = 2.97 \angle 18.5^\circ$$

$$\theta = (\theta_v - \theta_i) = 18.5 - 45 \Rightarrow \boxed{\theta = -26.5}$$

$$PF = \cos(\theta) \Rightarrow \boxed{PF = 0.894 = 89.4\%}$$

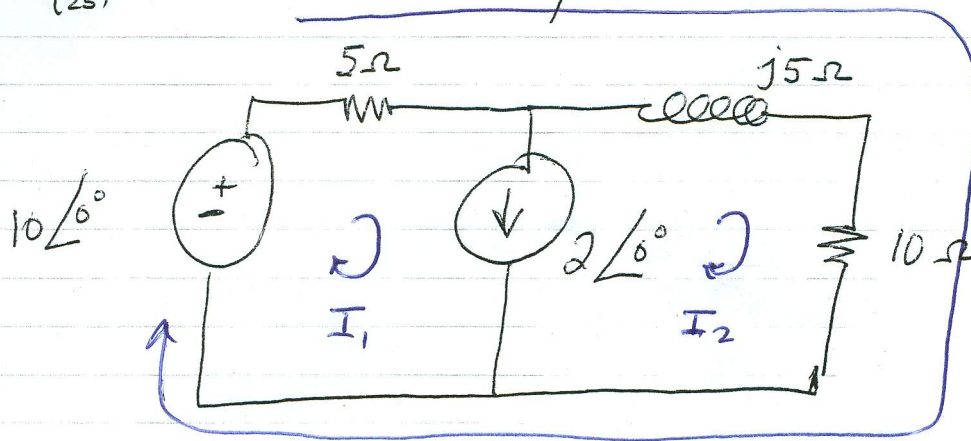Problem #3:
(25)

Find the Mesh Currents for the
Following Circuit.



$$(1) \quad 5I_1 + j5I_2 + 10I_2 - 10 = 0$$

$$(2) \quad I_1 - I_2 = 2$$

$$5I_1 + (10 + j5)I_2 = 10$$

$$I_1 = 2 + I_2$$

$$5(2 + I_2) + (10 + j5)I_2 = 10$$


$$10 + 5I_2 + (10 + j5)I_2 = 10$$

$$10 + (15 + j5)I_2 = 10$$

$$I_2 = \frac{0}{15 + j5}$$

$$\begin{aligned} I_2 &= 0 \text{ A} \\ I_1 &= 2 \text{ A} \end{aligned}$$

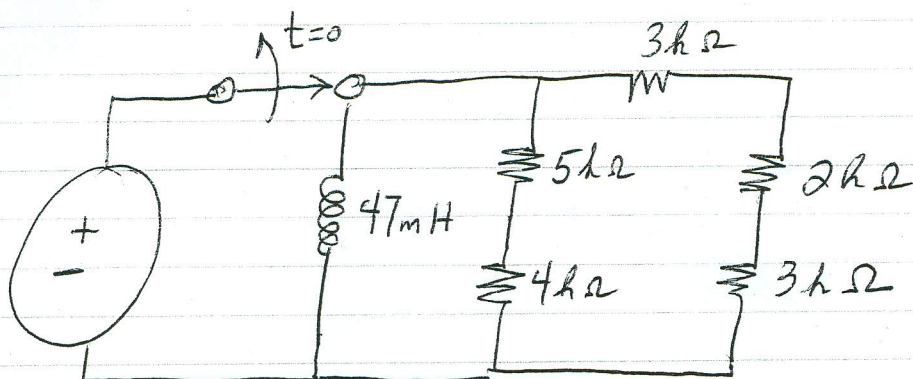Problem #4: Find the Time Constant for the given Circuit, after the Switch opens.
(15)



$$R_{TH} \Rightarrow 9//8$$

$$\tau = \frac{L}{R_{TH}} = \frac{47 \times 10^{-3}}{4.23 \times 10^3}$$


$$R_{TH} = \frac{72}{17} = 4.23 k\Omega$$

$$\tau = 1.11 \times 10^{-5} s$$

Problem #5:

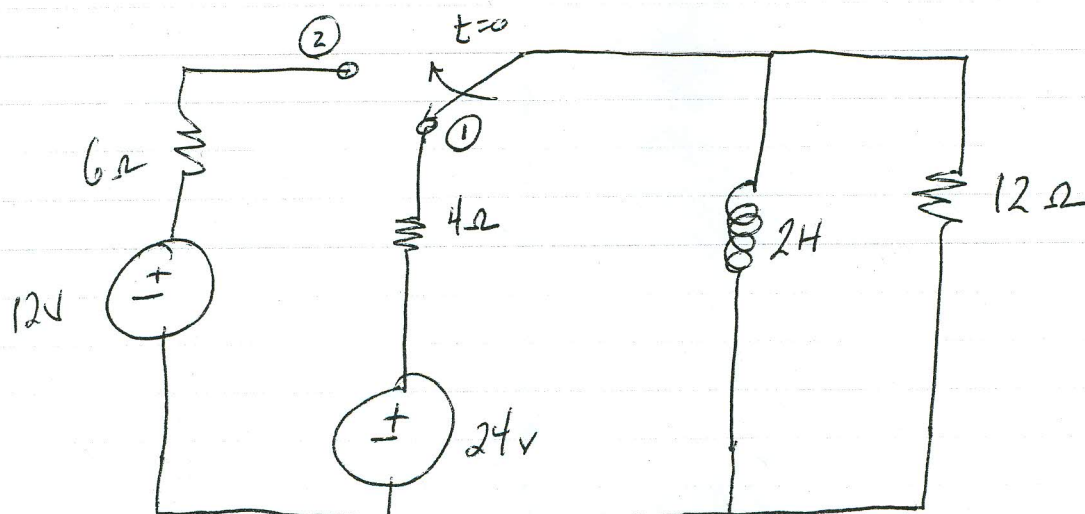(30)

The Circuit is in steady state @ $t=0$. Find $i(t)$ if the switch is moved from ① to ② @ $t=0$.



Before Switch Changes Position

$$i_L(0) = \frac{24}{4} = 6A$$


Note: in SS the inductor behaves like an inductor which "shorts" out the $12\Omega R$.

After Switch Changes Position

$$i_L(\infty) = \frac{12}{6} = 2A$$


Note: By some reasoning $12\Omega R$ is "shorted" out.

By Ph: $i_L(t) = i_L(\infty) - (i_L(\infty) - i_L(0))e^{-t/\tau}$

However: ~~~~

$$R_{TH} \Rightarrow 6//12 \Rightarrow R_{TH} = 4$$

$$\tau = \frac{L}{R} = \frac{2}{4} = 0.5s$$

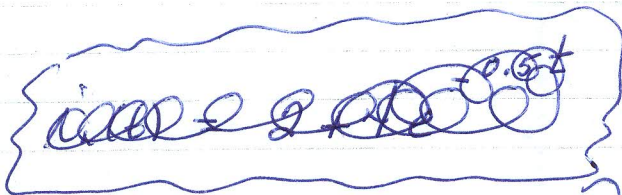~~~~

$$i_L(t) = 2 + 4e^{-2t}$$

Problem #6:

(10)

From the Perspective of the Engineer
Why Would you want to have the
Voltage & Current in Phase for A given
Circuit?

- ① Peaks at Same time
- ② No Reactive Power \rightarrow No Surges
- ③ Better Efficiency
- ④ "Backup" for Changes in Circuit Voltage
@ Surge