

LEHIGH UNIVERSITY

DEPT. OF ELECTRICAL & COMPUTER ENGINEERING

ECE 083 – SPRING 2013

EXAM #2


WEDNESDAY 27 MARCH 2013

NAME: _____

Tyler Brong.

75

#1

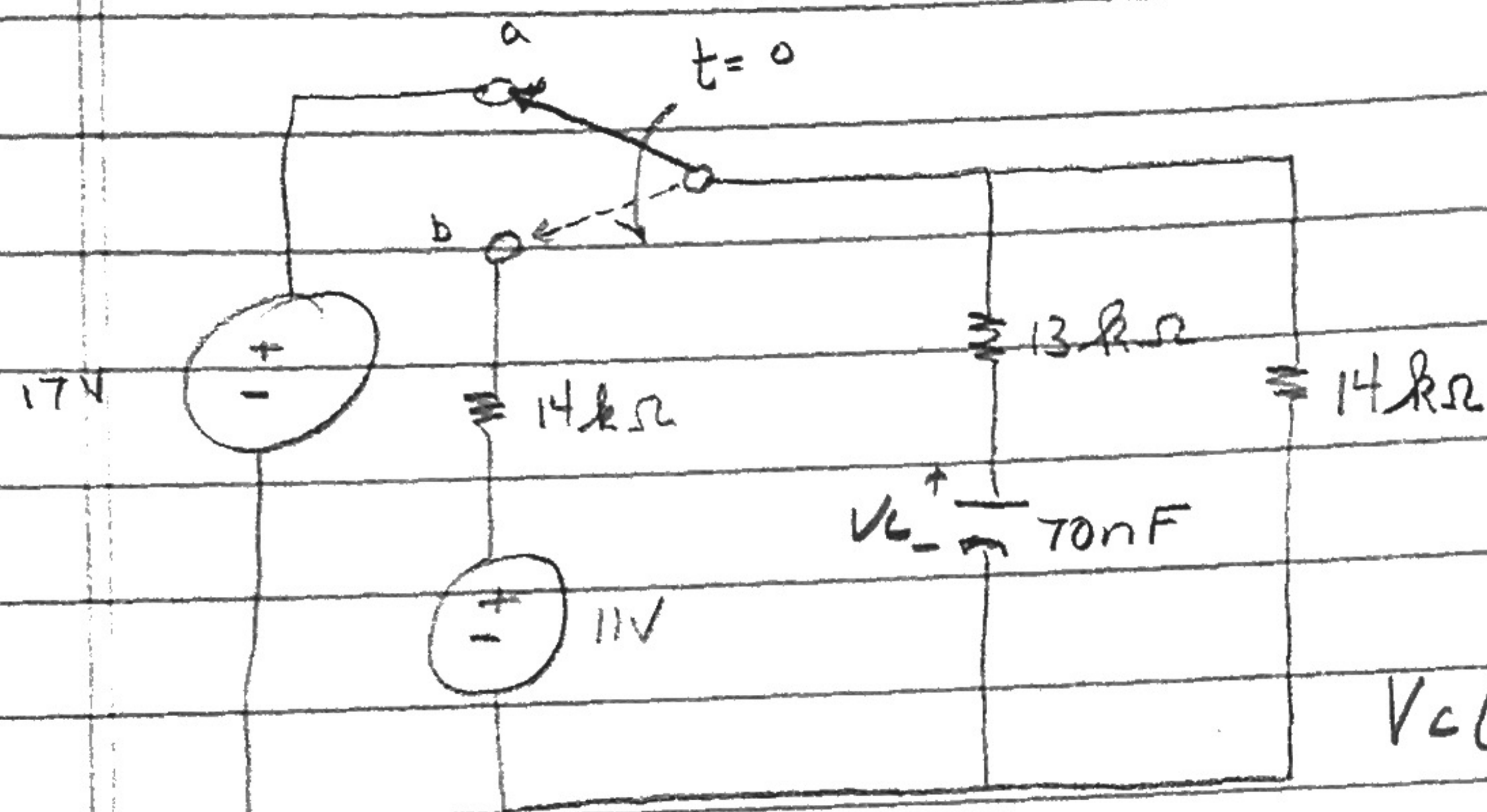For the Given Circuit Find $v_c(t)$ For $t > 0$.

NOTE: Circuit Has Been
@ a For A Long
Time Before it
Switches.

$$v_c(0) = v_s = 17 \text{ V}$$

$$\tau = RC$$

$$R_{eq} = (4550) (70 \times 10^{-9} \text{ F}) = 3.185 \times 10^{-4} \text{ s}$$

$$v_c(t) = I_s R + (v_i - I_s R) e^{-t/\tau}$$

$$11 + (17 - 11) e^{-t/3.185 \times 10^{-4}}$$

$$v_c(t) = 11 + 6 e^{-3139.716 t}$$

13

#2

Given $V_1(t)$, $V_2(t)$ and $V_3(t)$ Find $V_f(t)$

$$\text{If } V_f(t) = V_1(t) + V_2(t) + V_3(t)$$

$$V_1(t) = 40 \cos(60t - 30)$$

$$V_2(t) = 60 \cos(60t + 45)$$

$$V_3(t) = 90 \sin(60t - 75) \rightarrow 90 \cos(60t - 165^\circ)$$

$$V_1(t) = 40 \angle -30 \rightarrow 40 (\cos(-30) + j \sin(-30)) = 34.64 - 20j$$

$$V_2(t) = 60 \angle 45 \rightarrow 60 (\cos(45) + j \sin(45)) = 42.42 + j42.42$$

$$V_3(t) = 90 \angle -165 \rightarrow 90 (\cos(-165) + j \sin(-165)) = -86.93 - j23.29$$

$$\text{adding them} \rightarrow -9.87 - j.87$$

$$\sqrt{(-9.87)^2 + (-.87)^2} = 9.908$$


$$\tan^{-1}\left(\frac{-.87}{-9.87}\right) = 5.037$$

$$9.908 \cos(60t + 5.037) = V_f(t)$$

25

Answer → Oh Back

#3 For the Given Circuit Find $V_o(t)$.

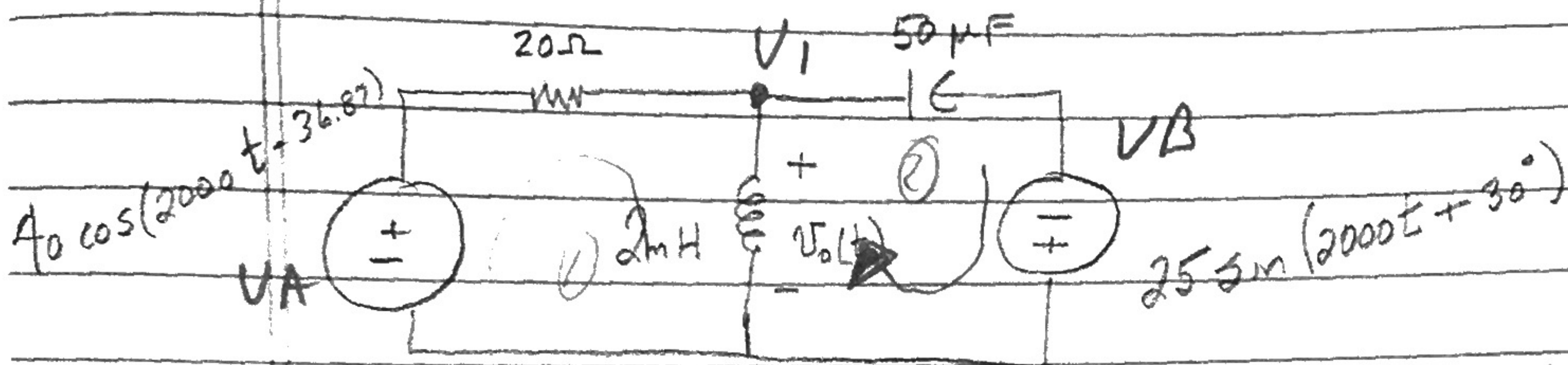

$$40 \cos(2000t - 36.87^\circ)$$

$$= 40 \angle -36.87^\circ$$

$$= 31.99 - j24$$

$$25 \sin(2000t + 30^\circ)$$

$$= 25 \angle -60^\circ$$

$$12.5 - j21.65$$

$$\text{total } V_{in} \text{ across } \text{loop} = 44.5 - j45.65 = 63.75 \angle -45.73^\circ$$

$$Z_{eq} \rightarrow 20 \Omega, j(2 \times 10^{-3})(2000), j\left(\frac{1}{(2000)(50 \times 10^{-6})}\right)$$

$$= 20 + j4 + j10 = 20 + j14$$

$$V_o(t) = 44.5 \cos(2000t - 45.73^\circ)$$

Solve for V_1

Node

$$\frac{V_1 - V_A}{20} + \frac{V_1}{j4} + \frac{V_1 + V_B}{-j10} = 0$$

$$\frac{V_1 - (31.99 - j24)}{20} + \frac{V_1}{j4} + \frac{V_1 + (12.5 - j21.65)}{-j10} = 0$$

$$V_1 \left(\frac{-31.99 + j24}{20} + \frac{1}{j4} + \frac{12.5 - j21.65}{-j10} \right) = 0$$

$$V_1 - 1.597 - j24 + \frac{V_1}{j4} + V_1 + 1.25j \angle 30^\circ$$

$$1.08 + j.625$$

$$V_1 - .517 - j23.375 + \frac{V_1}{j4} = 0$$

$$V_1 = j4(-.517 - j23.375) =$$

Back

$$4 \angle 90 \quad (23.38 \angle 88.7324)$$

$$93.522 \angle 178.7324 = V_0$$

$$V_0 = 93.522 \cos(2000t + 178.7724)$$

#4


For the Circuit Showed $i(t) = 1.25 \overset{\cos}{(5t - 15^\circ)} \text{ A (RMS)}$

a) What is the value of the complex Power

Associated with the Source if $R = 20 \Omega$ & $L = 3 \text{ H}$?

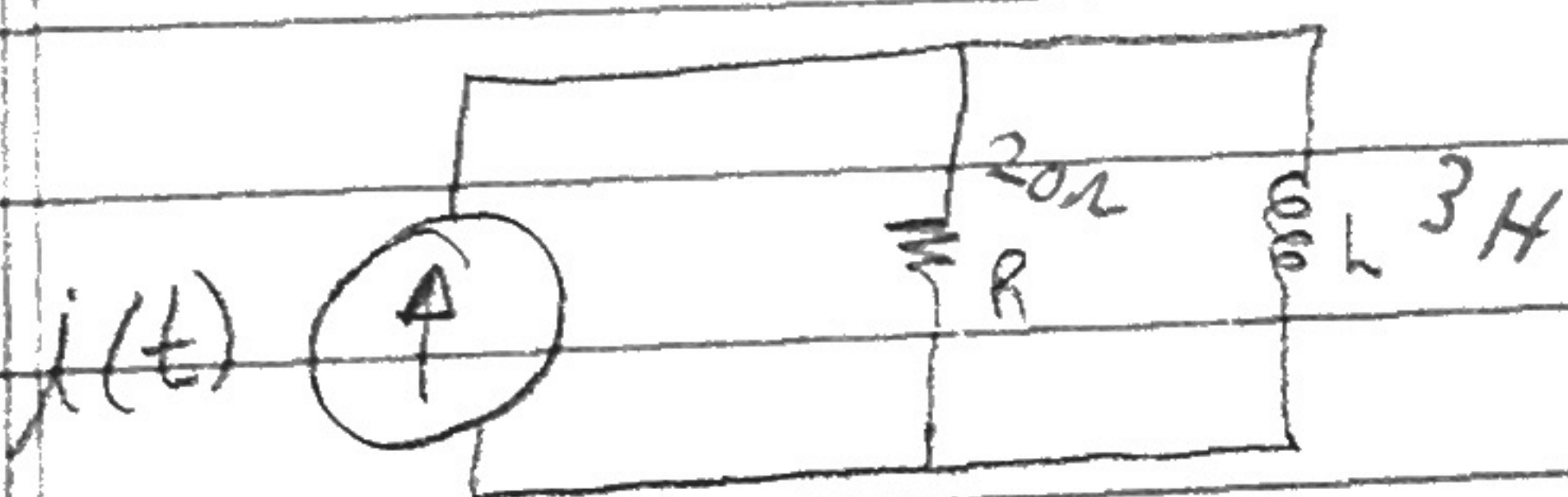b) What are the values of R & L if the Power

Associated with the Source is: $S = 16.57 \angle 45^\circ$?



$$S = Q + P$$

So, Find $Q + P$ for part A

a) Impedance $|Z| = 15j$

$$Z_{eq} = \frac{1}{20\Omega} + \frac{1}{j15\Omega} = \frac{1}{Z_{eq}} = 20 + j15 \Omega$$

$$V = IZ \rightarrow 1.25 \angle 15^\circ (20 + j15) \rightarrow 1.25 \angle 15^\circ (25 \angle 36.86^\circ)$$

$$V = 31.25 \angle 51.86^\circ$$

$$P = V_{rms} I_{rms} \cos(\theta_v - \theta_i) \rightarrow (31.25)(1.25) \cos(51.86^\circ - 15^\circ) = 31.25 \text{ Watts}$$

$$Q = V_{rms} I_{rms} \sin(\theta_v - \theta_i) = 23.432 \text{ VAR}$$

$$S = 31.25 + j23.432 \text{ V.A}$$

$$b) 16.57 \angle 45^\circ = P + Q$$

$$1.25(R + jL)$$

We know R will be Real Power and Q will be Reactive Power

$$\text{So, } 16.57 \angle 45^\circ \rightarrow 11.716 + j11.716$$

$$\text{Real} \rightarrow 11.716 = V_{rms} I_{rms} \cos(\theta) \rightarrow V_{rms} = 13.255 \text{ V}$$

$$\text{Reactive} \rightarrow 11.716 = V_{rms} I_{rms} \sin(\theta) \rightarrow$$

Back

$$\frac{RL}{R+L} = Z$$

$$S = P + Q$$

$$P = (I)^2 (Z) \cos(\theta_v - \theta_i)$$

$$Q = (I)^2 (Z) \sin(\theta_v - \theta_i)$$

$$= 1.25^2 (Z) \cos(45) = 11.5716$$

$$= [1.25]^2 (Z) \sin(45) = 11.5716 \text{ s}$$

$$10.604 = Z = \frac{RL}{R+L}$$

$$10.604 R + 10.604 L = RL$$

$$Z = \omega L$$

$$L = \frac{Z}{\omega}$$

$$R = 10.604 \Omega$$

$$L = 2.1208 \text{ H}$$