
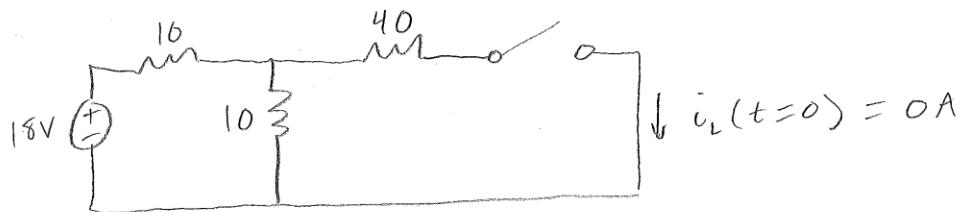


1.

Snapshot just before switch closes:

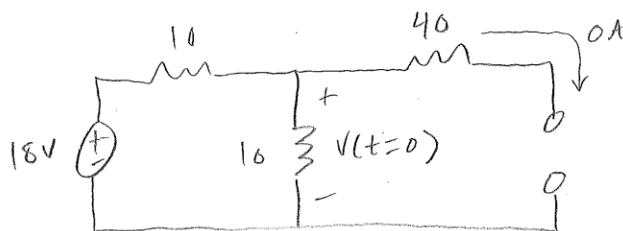


Just after switch closes:



Current thru inductor can't change instantaneously so it's going to act like an open circuit so that no current can flow thru it


$$V(t=0) = 18V \cdot \frac{10}{10+10} = 9V$$

At $t = \infty$:

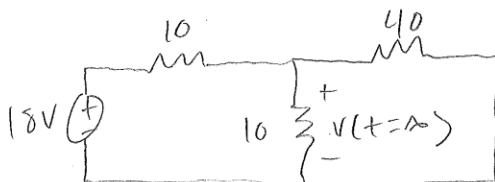

$$V(t=\infty) = 18V \cdot \frac{(10//40)}{(10//40)+10} = 8V$$

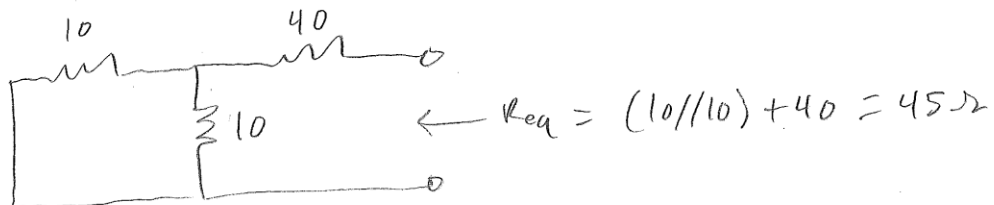To find τ , look at the circuit for $t \geq 0$ from the perspective of the inductor. Zero-out any independent sources



$$\tau = \frac{L}{R_{eq}} = \frac{25\text{H}}{45\ \Omega}$$


$$v(t) = v(t=\infty) + [v(t=0) - v(t=\infty)] e^{-t/\tau} \text{ V}$$

$$v(t) = 8 + (9-8) e^{-1.8t} \text{ V}$$

$$v(t) = 8 + e^{-1.8t} \text{ V}$$

$$2. \quad X_C = \frac{1}{\omega C} = 10 \Omega$$


$$X_L = \omega L = 10 \Omega$$

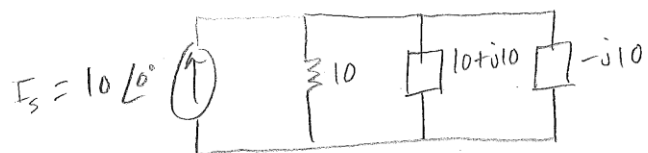

$$z_{eq} = 10 // (10 + j10) // (-j10) = 6 - j2$$

$$V_{10\Omega} = I_s z_{eq} = 60 - j20 \approx 63.24 \cos(1000t - 18.43^\circ) \text{ A}$$

3.

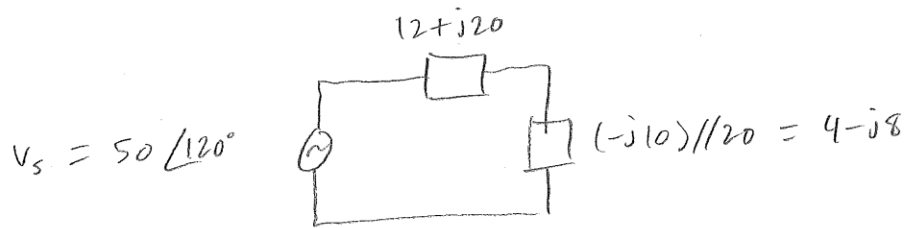


$$Z_{eq} = 12 + j20 + 4 - j8 = 16 + j12$$

$$I_s = \frac{V_s}{Z_{eq}} = 2.5 \cos(\omega t + 83.13^\circ) \text{ Arms}$$

$$S = \frac{|V_s|^2}{Z_{eq}^*} = \frac{50^2}{16 - j12} = 100 + j75$$


4. Want initial capacitor voltage to be 6V

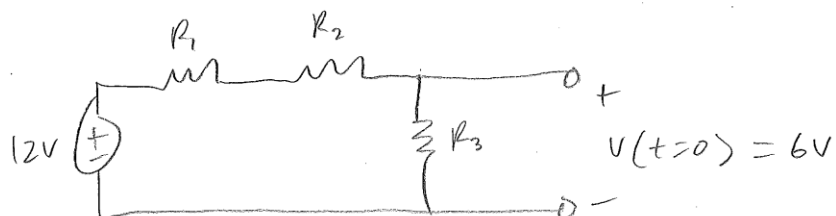

Constraint 1

$$6V = 12V \cdot \frac{R_3}{R_1 + R_2 + R_3}$$

Final capacitor voltage needs to be 10V

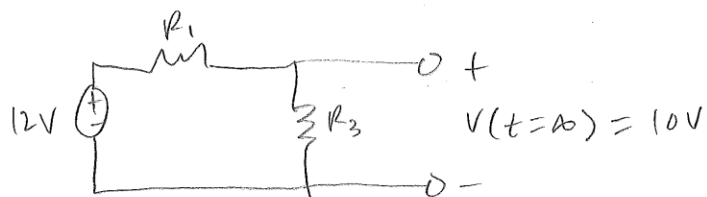


$$10V = 12V \cdot \frac{R_3}{R_1 + R_3}$$

constraint 2

$$5\tau = 10\text{ms} ; \tau = 2\text{ms} = R_{eq}C$$

Find R_{eq} :

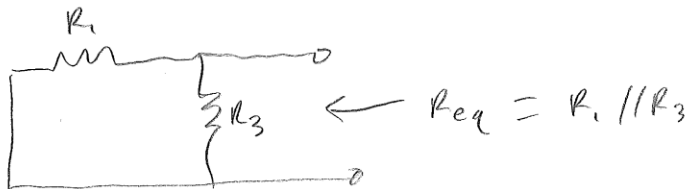

$$2\text{ms} = (R_1 \parallel R_3)C \quad \text{constraint 3}$$

From constraint 2, $R_3 = 5R_1$

Plugging this into constraint 1, $R_2 = 4R_1$

Say $R_1 = 1\text{k}\Omega$, then $R_2 = 4\text{k}\Omega$, $R_3 = 5\text{k}\Omega$

From constraint 3, $C = \frac{2 \times 10^{-3}}{(R_1 \parallel R_3)} = \frac{2 \times 10^{-3}}{3/2500} = 2.4\mu\text{F}$

